

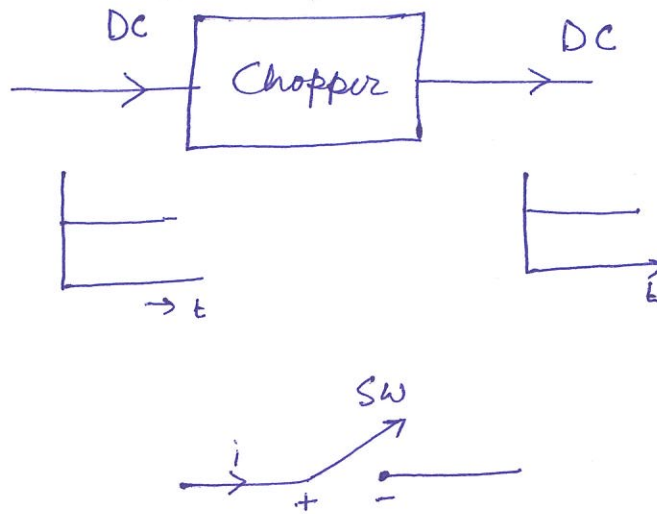


# DC-DC Converters (Choppers)

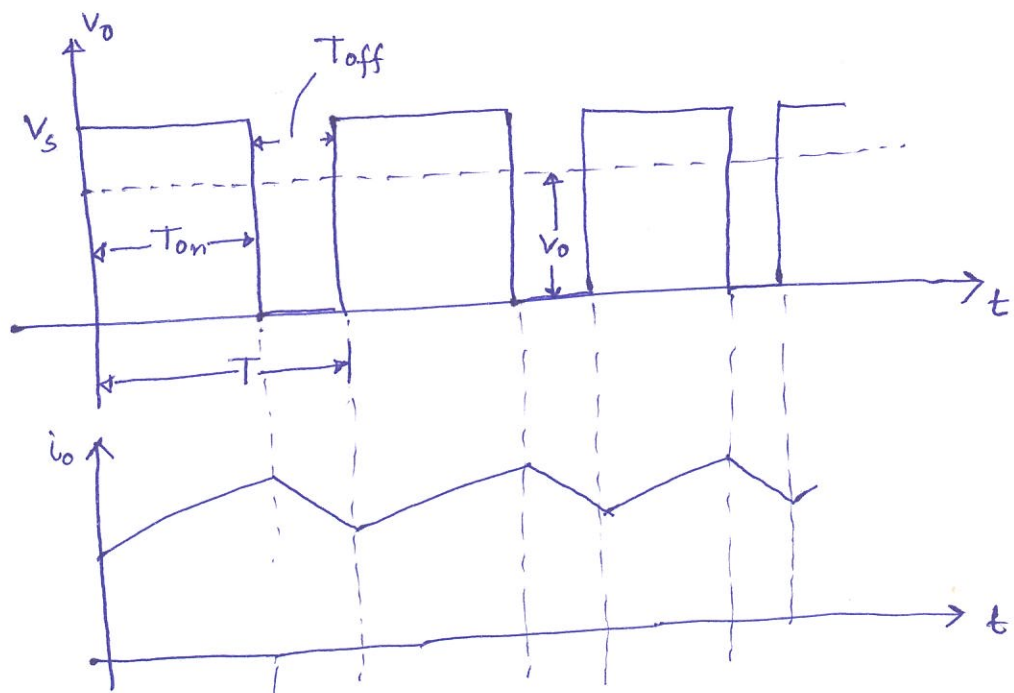

## Step down Chopper: (Buck Converter)

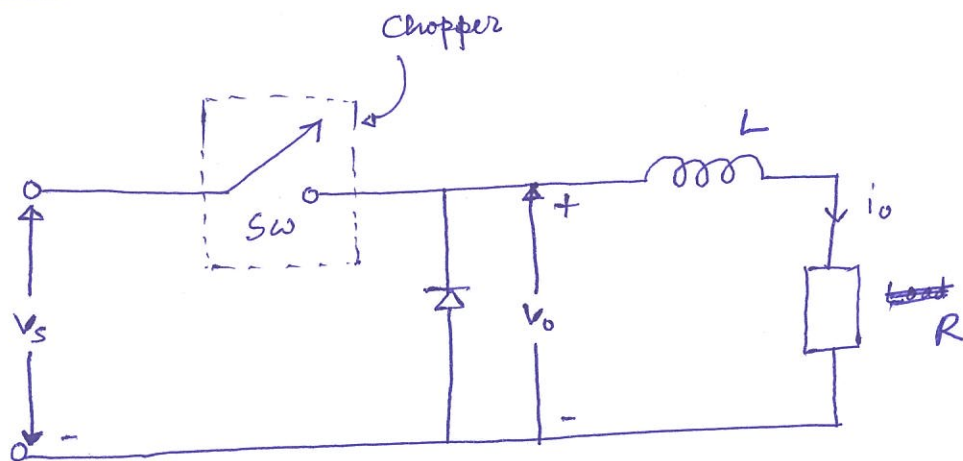

$$V_o = \frac{T_{on}}{T_{on} + T_{off}} V_s = \frac{T_{on}}{T} V_s = \alpha V_s$$

$T_{on}$  = on-time       $T_{off}$  = off-time

$T = T_{on} + T_{off}$  = chopping period

$\alpha = \frac{T_{on}}{T}$  = duty cycle

$V_o = f \cdot T_{on} \cdot V_s$        $f = \frac{1}{T}$  = chopping frequency

### Control Strategy:

#### # Constant frequency System:

$T_{on}$  is varied but  $f$  is kept constant.



adjustment of pulse width  $\rightarrow$  pulse-width-modulation (PWM)

#### # Variable frequency System

Chopping frequency  $f$  is varied.

Or






- $T_{on}$  is kept constant
- $T_{off}$  " " "

$\rightarrow$  frequency modulation.


### PWM vs FM

- Filter design is difficult
- Possibility of interference with signalling and telephone lines.
- Large off-time in frequency modulation scheme may make the load current discontinuous which is undesirable.

## Step-up Choppers!

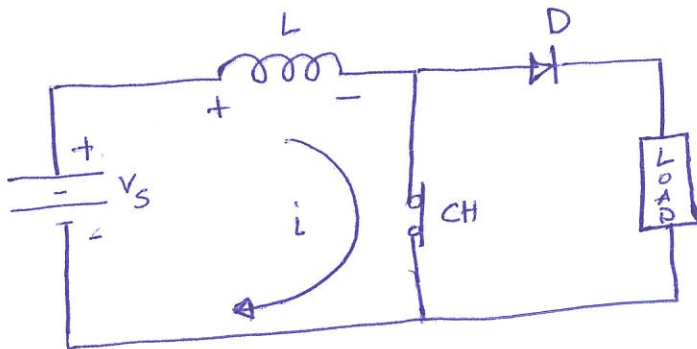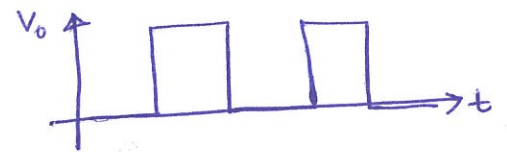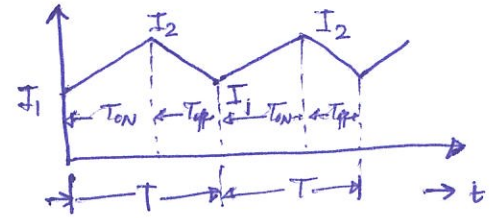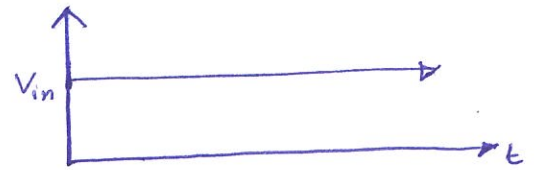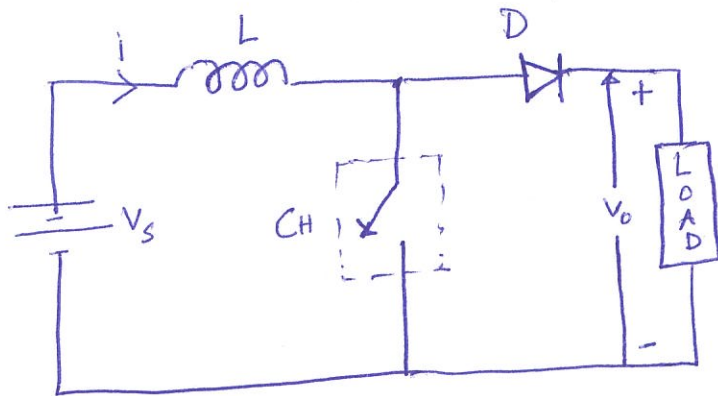
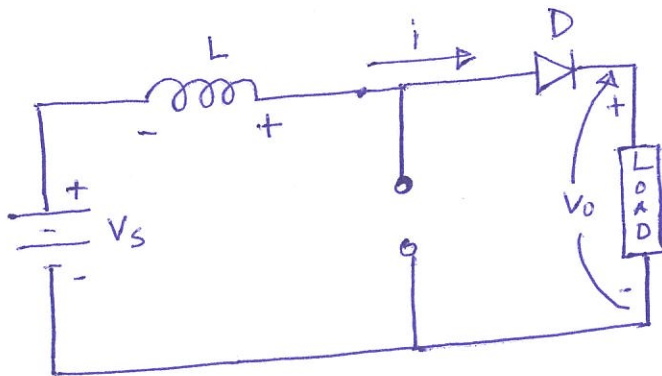
$$\rightarrow \begin{cases} V_L = V_s, & V_o = 0 \end{cases}$$



$$\rightarrow \begin{cases} V_L = V_o - V_s \\ V_o = V_s + L \left( \frac{di}{dt} \right) \end{cases}$$

Assuming linear variation of output current, the energy input to the inductor from the source, during the period  $T_{on}$  is

$$W_{in} = (\text{voltage across } L) \cdot (\text{average current through } L)$$

$$= V_s \left( \frac{I_1 + I_2}{2} \right) T_{on}$$

During the time  $T_{off}$ , the chopper is off, the energy released by inductor to the load is

$$W_{off} = (\text{voltage across } L) (\text{average current through } L) T_{off}$$


$$= (V_o - V_s) \left( \frac{I_1 + I_2}{2} \right) T_{off}$$

Considering the system to be lossless,

$$V_s \left( \frac{I_1 + I_2}{2} \right) T_{on} = (V_o - V_s) \left( \frac{I_1 + I_2}{2} \right) T_{off}$$

$$V_o = V_s \frac{T}{T - T_{on}} = V_s \frac{1}{1 - \alpha}$$

Q.

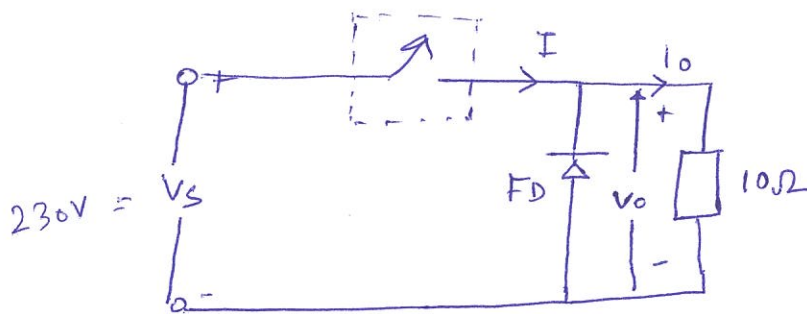

Consider voltage drop of 2V across chopper when it is on, for a duty cycle of 0.4, Calculate

- average and rms values of output voltage
- chopper efficiency

Q.

A step-up chopper has input voltage of 220V and output voltage of 660V. If the non-conducting time of thyristor-chopper is 100μs, Compute the pulse width of output voltage.

In case, pulse width is ~~halved~~ <sup>halved</sup> for constant frequency operation, find the new output voltage.